

# CprE 381, Computer Organization and Assembly Level Programming

## Lab 1 Report

Student Name : Rafat Momin

***Submit a typeset pdf version of this on Canvas by the due date. Refer to the highlighted language in the lab document for the context of the following questions.***

[Part 1.c] Think of three more cases and record them in your lab report.

[Part 1.e] For labels 1, 7, 22, and 28, specify where (VHDL file and line number) these values are located – some will be found in more than one place. Also attempt to explain the functionality of each label as it occurs in the code

[Part 1.g.v] In your lab report, include a screenshot of the waveform. Describe, in plain English, any differences between what you expected and what the simulation showed.

[Part 1.h] In your lab report, include a screenshot of the waveform. Describe, in plain English, how your waveform matches the expected result (e.g., reference the specific cycles and times). In your submission zip file, provide the completed *TPU\_MV\_Element.vhd* file in a folder called 'MAC'.

[Part 3.a] Draw the truth table, Boolean equation, and Boolean circuit equivalent (using only two-input gates) that implements a 2:1 mux. Include this in your lab report.

[Part 3.d] In your lab report, include a screenshot of the waveform. Make sure to label the screenshot with which module it is testing.

[Part 3.e] Again, in your lab report, include a labeled screenshot of the waveform showing the dataflow mux implementation working.

[Part 4] Include a waveform screenshot and corresponding description demonstrating it is working correctly.

[Part 5.b] Include a waveform screenshot and description in your lab report.

[Part 6.a] A full adder takes three single-bit inputs and produces two single-bit outputs – a sum and carry for the addition of the three input bits. Draw the truth table, Boolean equation, and Boolean circuit equivalent (using only two-input gates) that implements a 1-bit full adder. Include this in your report.

[Part 6.c] Then draw a schematic of the intended design, including inputs and outputs and at least the 0, 1, N-2, and N-1 stages. Include this in your report.

[Part 6.d] Include an annotated waveform screenshot in your write-up.

[Part 7.a] Draw a schematic (don't use a schematic capture tool) showing how an N-bit adder/subtractor with control can be implemented using only the three main components designed in earlier parts of this lab (i.e., the N-bit inverter, N-bit 2:1 mux, and N-bit adder). How is the 'nAdd\_Sub' bit used? Include this in your report.

[Part 7.c] Provide multiple waveform screenshots in your write-up to confirm that this component is working correctly. What test-cases did you include and why?

```
-- Test case 3:
-- Perform average example of an input activation of 3 and a partial sum of 25. The weight is still 10.
s_iX  <= x"04"; -- 3 in hexadecimal
s_iW  <= x"00"; -- Not strictly necessary, but this makes the testcases easier to read
s_ildW <= '0';  -- Make sure we don't continue to load.
s_iY  <= x"19"; -- 25 in hexadecimal
wait for gCLK_HPER*2;
wait for gCLK_HPER*2;
-- Test case 4:
-- Perform average example of an input activation of 3 and a partial sum of 25. The weight is still 10.
s_iX  <= x"05"; -- 3 in hexadecimal
s_iW  <= x"00"; -- Not strictly necessary, but this makes the testcases easier to read
s_ildW <= '0';  -- Make sure we don't continue to load.
s_iY  <= x"19"; -- 25 in hexadecimal
wait for gCLK_HPER*2;
wait for gCLK_HPER*2;
-- Test case 5:
-- Perform average example of an input activation of 3 and a partial sum of 25. The weight is still 10.
s_iX  <= x"06"; -- 3 in hexadecimal
s_iW  <= x"00"; -- Not strictly necessary, but this makes the testcases easier to read
s_ildW <= '0';  -- Make sure we don't continue to load.
s_iY  <= x"19"; -- 25 in hexadecimal
wait for gCLK_HPER*2;
wait for gCLK_HPER*2;

wait;
end process;
```

## Part 1c

I added 3 more test cases in my testbench file.

### 1e

#### Label 1:

**File:** TPU\_MV\_Element.vhd

The clock signal **iCLK** is first declared in the entity port declaration.

- **Functionality:** This label refers to the clock input for the processing element, which is critical for controlling the timing of all synchronous operations within the module.

#### Label 7 :

- **File:** Adder.vhd
  - **oC:** oC is declared on line 16 in the adder entity where it is defined as an output port.
- **Functionality:** Label 7 likely refers to the actual addition operation that produces the output oC

#### Label 22 :

- **File:** TPU\_MV\_Element

The s\_w is first instantiated within the vhd file in line 77.


- **Functionality:** The signal s\_W would be used within the module to store weight values, potentially coming from a weight register (g\_Weight) that latches weights based on a load control signal.

#### Label 28 :

- **File:** TPU\_MV\_Element.vhd


Near the outputs of complex operations or at the end of processing chains.

 **Functionality:** Represents the final or intermediate output from a processing stage, potentially acting as a stored result or a state value passed on for additional computation or output.




#### Part 1.g.v


I added three more test cases(3,4,5). I changed the value of s\_iX to 4,5,6 initially. Afterward, I got these values 65,75,85. Because the multiplier weight value is 10, 4,5,6 multiplies with 10, and the adder adds the value 25. While starting the simulation, I got an unexpected value instead of 55. Because inside the TPU\_MV\_Element.vhd file it was not initialized to the right value. I changed that and then got my expected results.

 

Part 1.h

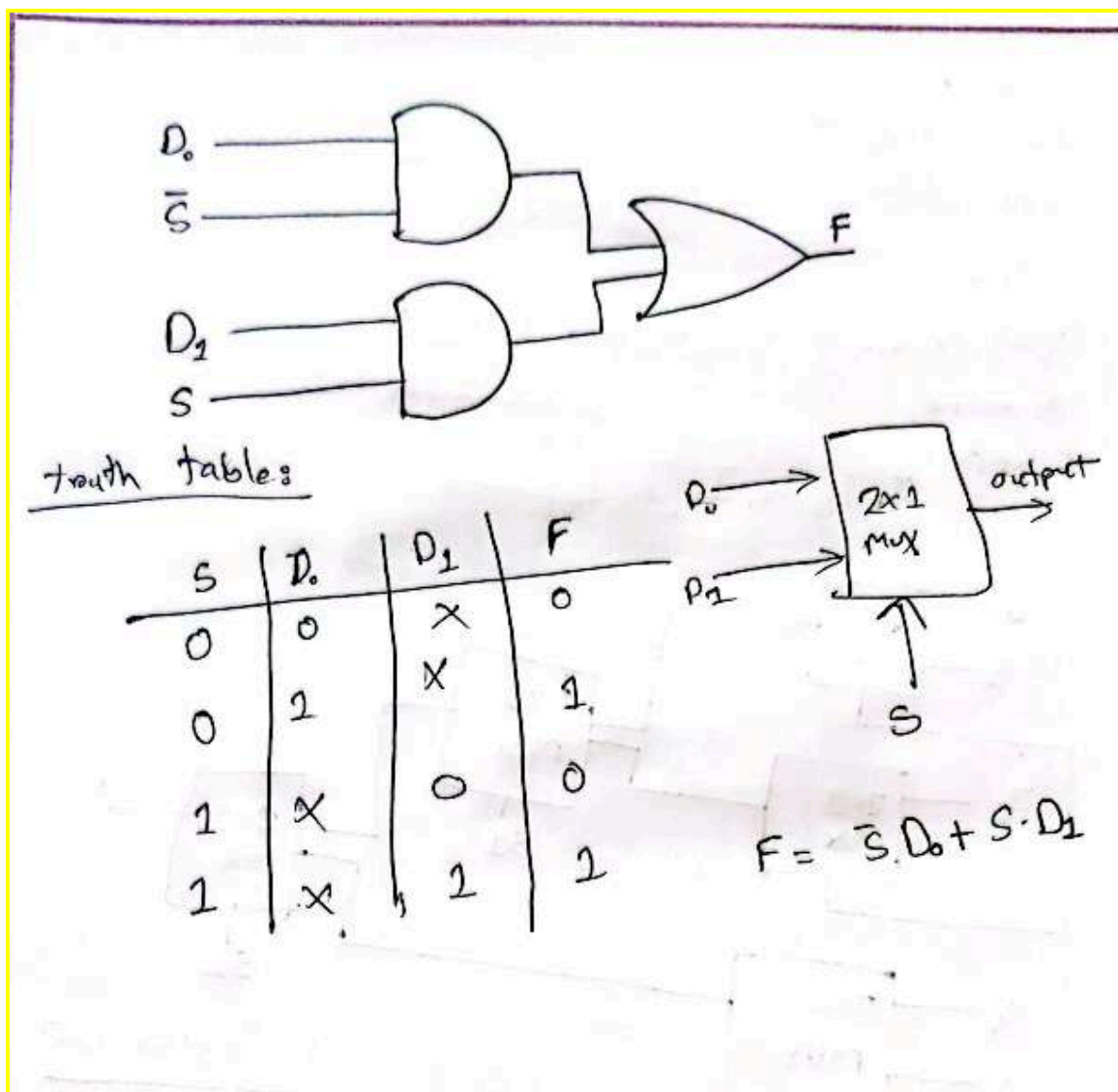

Part 3A

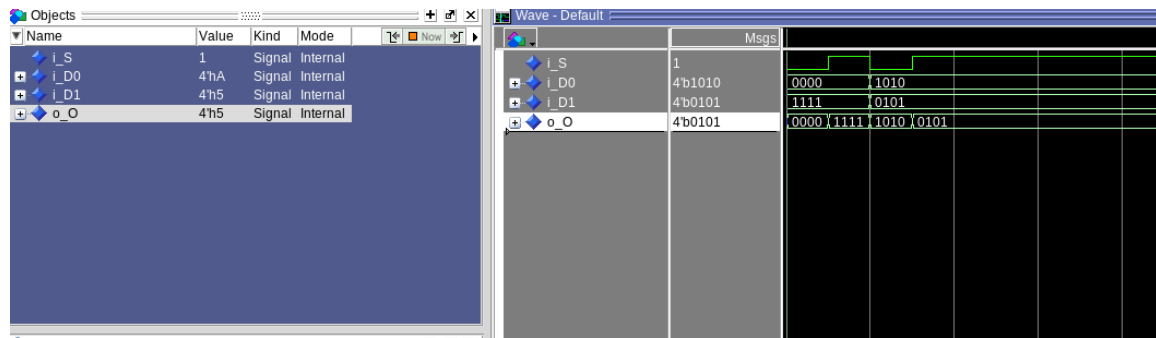

### Part 3d

#### Test Case 1: Select i\_D0

- Initial Condition: i\_S = '0' (select signal for i\_D0), i\_D0 = "0000", i\_D1 = "1111".
- Expectation: When i\_S is '0', the multiplexer should select i\_D0. Thus, o\_O should be equal to i\_D0 which is "0000".
- Waveform Annotation: Highlight the portion of the waveform where i\_S changes to '0' and verify that o\_O changes to "0000" simultaneously. Annotate this change to illustrate that the multiplexer is correctly selecting i\_D0.

#### Test Case 2: Select i\_D1

- Condition: After 10 ns, i\_S changes to '1' (select signal for i\_D1).
- Expectation: With i\_S now '1', o\_O should switch to "1111", matching the value of i\_D1.
- Waveform Annotation: Mark the timeline where i\_S switches to '1'. Show that o\_O updates to "1111" at this point, confirming the mux's response to the select signal.

#### Test Case 3: Change Inputs While Selector is '0'


- Condition: Inputs i\_D0 and i\_D1 change to "1010" and "0101", respectively, while i\_S remains '0'.
- Expectation: Since i\_S is still '0', o\_O should reflect the new value of i\_D0, which is "1010".
- Waveform Annotation: Illustrate the change in i\_D0 and i\_D1 and ensure o\_O follows i\_D0's change to "1010". This demonstrates that the mux continues to hold the correct selection despite changes in inputs.

#### Test Case 4: Toggle Selector After Changing Inputs


- Condition: i\_S toggles to '1' after the input changes.
- Expectation: As i\_S switches to '1', o\_O should now match i\_D1's value, "0101".
- Waveform Annotation: Display the point where i\_S switches back to '1'. Confirm that o\_O changes to "0101", indicating the mux is dynamically responding to both selector and input changes.



### Part3e

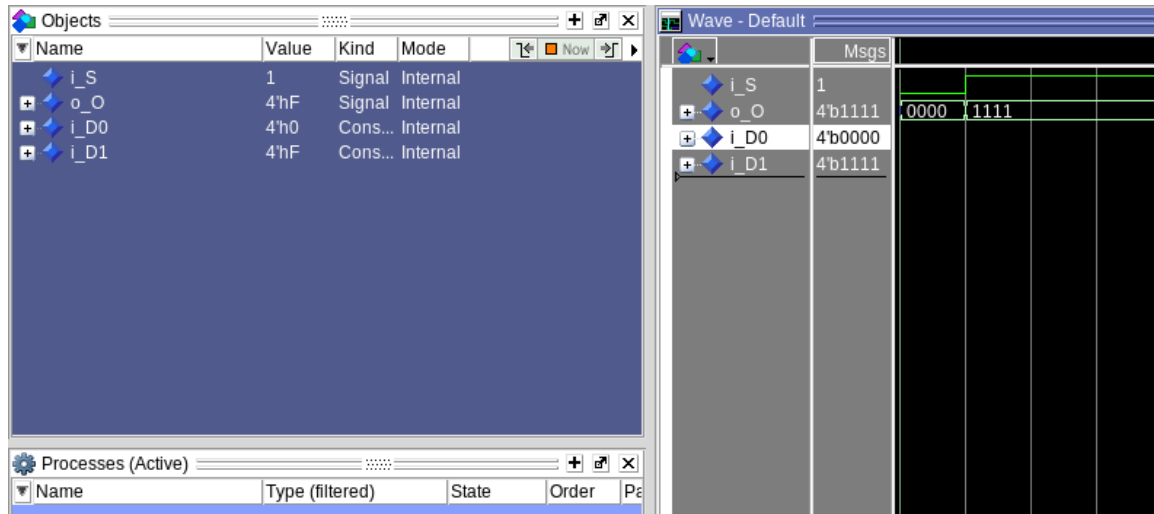

### Part3e

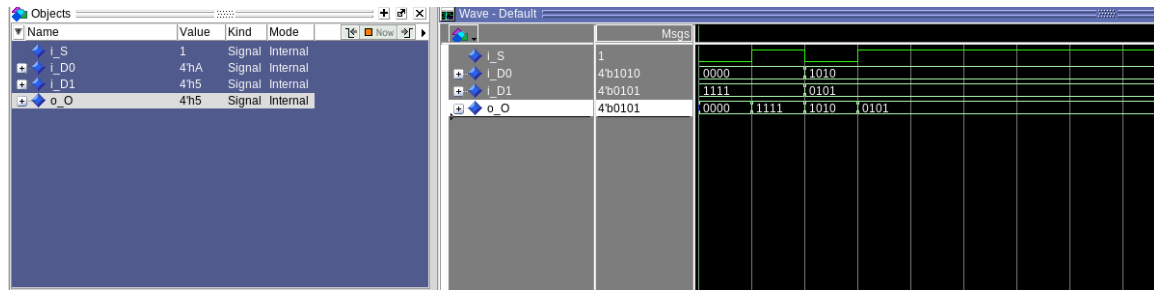

### Test Case 1: Select i\_D0


- Scenario Setup:
  - Selector Signal (i\_S): Initialized to '0' to select the first input, i\_D0.
  - Input Values: i\_D0 = "0000" and i\_D1 = "1111".
- Expected Output: When i\_S is '0', the output o\_O should match the value of i\_D0, which is "0000".
- Waveform Annotation: Highlight the segment where i\_S is '0'. Annotate the waveform to show that o\_O correctly reflects "0000", confirming that the multiplexer is selecting the first input (i\_D0). The annotation could read: "Selector is 0, output matches i\_D0: 0000."

### Test Case 2: Select i\_D1

- **Scenario Setup:**
  - **Selector Change:** After 10 ns, *i\_S* changes to '1' to select the second input, *i\_D1*.
- **Expected Output:** With *i\_S* set to '1', *o\_0* should switch to match *i\_D1*, which is "1111".
- **Waveform Annotation:** Mark the instance when *i\_S* transitions to '1'. Note on the waveform that *o\_0* updates to "1111" at this point. This annotation helps illustrate the multiplexer's dynamic response to the select signal changing. You might note: "Selector changes to 1, output updates to match *i\_D1*: 1111."
 
#### Part4

The waveform screenshot provided illustrates the correct functionality of the N-bit 2:1 multiplexer, designed using a structural VHDL approach with a generate for statement. The testbench effectively validates the multiplexer's ability to select between two N-bit input vectors (*i\_D0* and *i\_D1*) based on the value of the selection signal (*i\_S*).



#### Part5b


##### Test Case 1: All Zeros Input

- **Scenario Setup:**
  - **Input (*i\_A*):** Initialized to all zeros ("00000000000000000000000000000000").
- **Expected Output:** When *i\_A* is all zeros, the output *o\_F* should be all ones ("11111111111111111111111111111111").
- **Waveform Annotation:** Highlight the portion of the waveform where *i\_A* is all zeros. Note on the waveform that *o\_F* correctly reflects all ones, confirming that the ones complementor is functioning as expected. The annotation might read: "Input is all zeros, output correctly shows all ones as per ones complement operation."

##### Test Case 2: All Ones Input

- **Scenario Setup:**

- **Input (i\_A):** Changed to all ones ("11111111111111111111111111111111").
- **Expected Output:** With i\_A set to all ones, o\_F should switch to all zeros ("000000000000000000000000000000").
- **Waveform Annotation:** Mark the instance when i\_A transitions to all ones. Note on the waveform that o\_F updates to all zeros at this moment. This annotation helps illustrate the ones complementor's response to the input change. You could note: "Input changes to all ones, output correctly flips to all zeros as expected."

 

Part 6a





(c) stage 0 (0th bit)

stage 1 (1st bit)

stage 2  $N-2$

stage  $N-1$  (last bit)

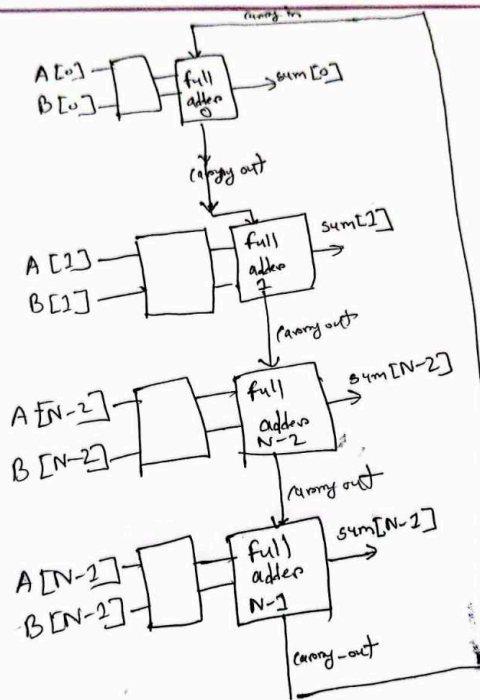

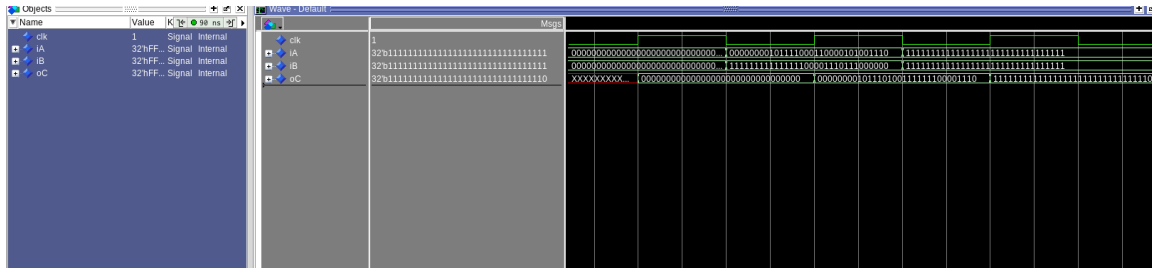

## Part6d

Initial State (0ns to 20ns):


- Inputs: **iA** and **iB** are both set to zero (00000000000000000000000000000000).
- Output: **oC** should also be zero (00000000000000000000000000000000), reflecting the correct sum of the inputs.
- Clock: Observes a toggle from '0' to '1' every 10ns, simulating a typical clock signal.

First Input Change (20ns to 40ns):


- Inputs:
  - **iA** is set to 0000000000000101111101110011010010 (binary for 12345678).
  - **iB** is set to 11111111111111111111111111111111000001001000 (binary for -123456 using two's complement).
- Output: **oC** should display the sum of these two numbers in binary, showcasing the adder's capability to handle both positive and negative values.

Overflow Condition (40ns onwards):


- Inputs: Both **iA** and **iB** are set to maximum negative values (11111111111111111111111111111111), intending to test the overflow condition.
- Output: **oC** will reflect the overflow condition, potentially showing either the maximum or minimum possible value, depending on how overflow is managed within the Adder design.

 

Part7a

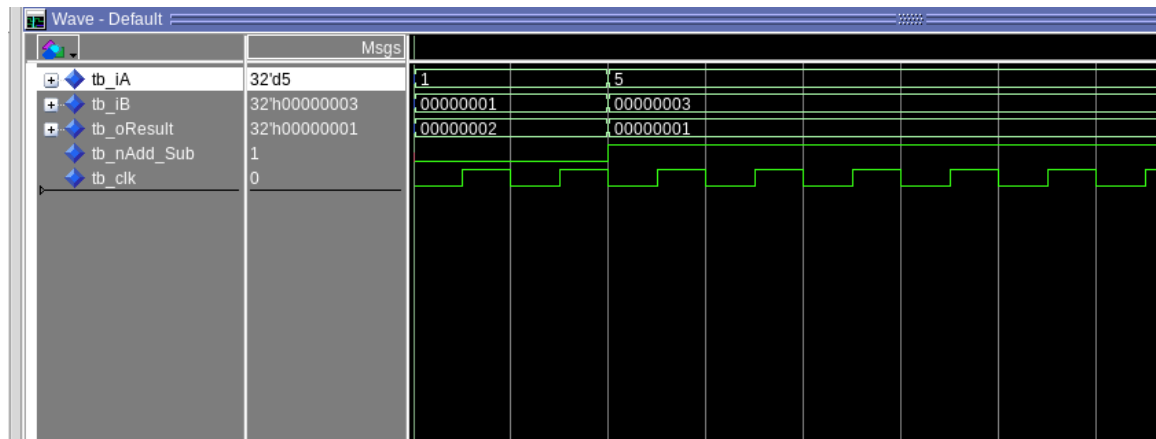

Part7c

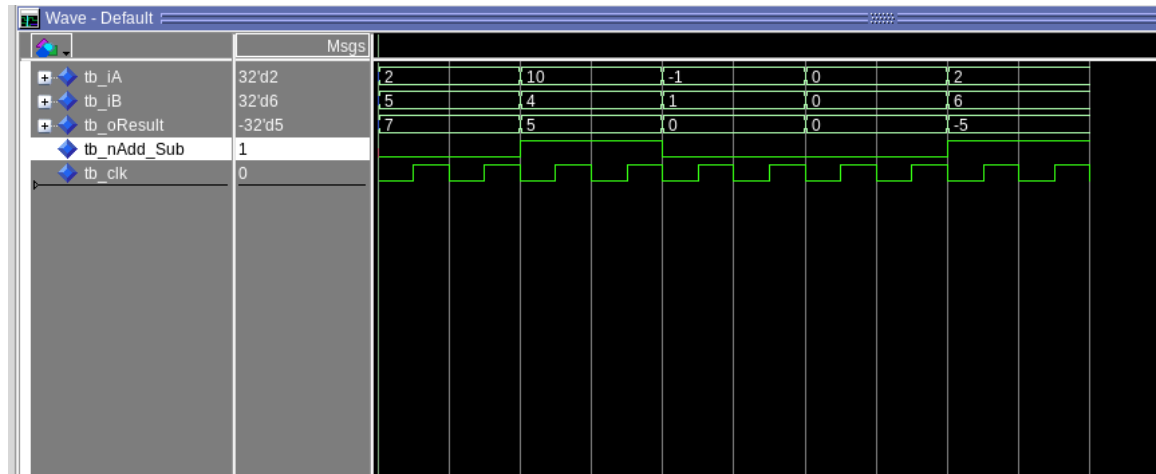

Part7c(in decimals)

## Waveform Annotation for Testbench 1 (Binary Format)

In this waveform from the first testbench (`adder_sub_tb.vhd`), we observe the following sequence:

### 1. Initial State:

- `iA` and `iB` are both initialized to binary `00000000000000000000000000000001`, which corresponds to the decimal value 1.
- The `nAdd_Sub` signal is set to '0', indicating an addition operation.
- The operation results in `oResult` being `00000000000000000000000000000010`, binary for 2, which is the correct output for the addition of 1 and 1.

### 2. Subsequent State:

- The inputs `iA` and `iB` transition to `00000000000000000000000000000101` (binary for 5) and `00000000000000000000000000000011` (binary for 3) respectively.
- The `nAdd_Sub` signal switches to '1', triggering a subtraction operation.
- The resulting `oResult` correctly displays `00000000000000000000000000000010` (binary for 2), validating the subtraction of 3 from 5.

## Waveform Annotation for Testbench 2 (Decimal Format)

The waveform from the second testbench (`adder2_sub2_tb2.vhd`) shows these key sequences:

### 1. Test 1: Addition (0ns to 20ns)

- Inputs: `iA` = 2, `iB` = 5
- Operation: Addition (`nAdd_Sub` = 0)
- Expected and observed result: `oResult` = 7 which correctly represents the addition of 2 and 5.

### 2. Test 2: Subtraction (20ns to 40ns)

- Inputs: `iA` = 10, `iB` = 4
- Operation: Subtraction (`nAdd_Sub` = 1)
- Expected and observed result: `oResult` = 6 which correctly captures the result of subtracting 4 from 10.

### 3. Test 3: Overflow Addition (40ns to 60ns)

- Inputs: `iA` = `0xFFFFFFFF`, `iB` = 1 (attempting to simulate overflow)
- Operation: Addition (`nAdd_Sub` = 0)
- Expected and observed result: `oResult` = 0 due to overflow, which is correctly handled by the simulator.

### 4. Test 4: Zero Addition (60ns to 80ns)

- Inputs: `iA` = 0, `iB` = 0
- Operation: Addition (`nAdd_Sub` = 0)
- Expected and observed result: `oResult` = 0, correctly reflecting the addition of zero and zero.

5. **Test 5: Negative Result Subtraction (80ns to 100ns)**

- Inputs: `iA` = 2, `iB` = 6
- Operation: Subtraction (`nAdd_Sub` = 1)
- Expected and observed result: `oResult` = -4, correctly showing the subtraction of 6 from 2 yielding a negative result.